

# **Explanation of the BM055 Circuit Schematic**

This document explains the BM055-based circuit schematic for the "Robot Controller v1.0" project.

Key Components and Connections:

- 1. BM055 Sensor (U5):
  - The central component in the schematic, likely used for motion or environmental sensing.
  - Contains power, ground, data communication, and interrupt pins.

#### 2. Power Connections:

- Operates on a 3.3V power supply (connected to the VDD pin).
- Includes decoupling capacitors (C24 and C25, 0.1 uF each) between the power supply and ground to reduce noise.

#### 3. Data Communication:

- SDI (Pin 10), SDO (Pin 9), and SCK (Pin 8): Likely used for SPI communication protocol.
- SDA (Pin 11) and SCL (Pin 12): Alternatively used for I2C communication protocol.

#### 4. Pull-up Resistors:

- R16 and R17 (10 kOhm each): Connected to the SDA and SCL lines for I2C communication.

# 5. Interrupt Pins:

- INT1 and INT2: Can trigger interrupts, but might be left unconnected (marked "NC").

#### 6. Unused Pins:

- INT3 and INT4: Marked as "NC," not connected in this design.

## 7. Decoupling Capacitors:

- Capacitors C24 and C25: Placed close to the sensor for stability and noise filtering.

## 8. Additional Resistors:

- R18 and R19: Marked as NC (not connected), serving as placeholders for future design changes.

## General Observations:

- The circuit is well-structured, demonstrating a professional design approach.
- This schematic, authored by Ruchira Thilan Manusinghe for Rise (Pvt) Ltd, embeds the BM055 sensor into a robot controller for sensing or environmental monitoring.

For further questions or modifications to the design, additional details can be provided upon request.