


Project: Robot Controller v1.0.PrjPcb			Author: <i>Ruchira Thilan Munasinghe</i>		
Title:			<div>Orise (Pvt) Ltd 400/B Galaha Road Peradeniya Sri Lanka</div> <div> Automating the future</div>		
Size: A4	Revision:				
Date: 27/06/2023	Time: 13:43:27	Sheet	of		
File: E:\ORISE\projects\Robot Controller\Electronic design\Robot Controller v1.0\6.BMP388.SchDoc					

Schematic Explanation for Sensor Interface

This schematic represents another part of the "Robot Controller v1.0" circuit, showing the integration of a BMP388 sensor module. Here's a detailed breakdown:

Key Components:

1. U7 (BMP388):

- This is a high-precision digital pressure sensor with I²C and SPI communication capabilities.
- Pins:
 - VDD (Pin 9): Connected to the 3.3V power supply.
 - VSS_1, VSS_3 (Pins 2, 8): Connected to the ground.
 - SCK (Pin 5): Clock line for SPI or I²C communication.
 - SDI (Pin 4): Data input line, shared for I²C (SDA) or SPI.
 - SDO (Pin 3): Data output, used in SPI communication.
 - CSB (Pin 1): Chip select pin to switch between SPI and I²C communication modes.

2. Capacitors (C27 and C28):

- Decoupling capacitors (0.1 μ F) placed close to the power pins (VDD and VSS) to stabilize the power supply and filter out high-frequency noise.

3. Pull-Up Resistors (R22, R23):

- R23 (10 k Ω): Pull-up resistor for the I²C data line (SDA), ensuring a proper logic high level when no device is driving the line.
- R22 (NC): Placeholder for future use or alternate configurations.

Key Connections:

1. Power Supply:

Schematic Explanation for Sensor Interface

- The sensor is powered by a stable 3.3V source connected to VDD.
- Ground pins are connected to ensure a common reference point.

2. Communication Lines:

- The SCL (clock) and SDA (data) lines support I²C communication, with pull-up resistors ensuring proper signal levels.
- Alternatively, the SCK and SDI/SDO pins enable SPI communication.

3. Chip Select (CSB):

- This pin is likely configured for selecting communication protocols:
 - Low for SPI mode.
 - High or floating for I²C mode.

Observations:

- The schematic ensures reliable communication between the BMP388 and a microcontroller using either SPI or I²C protocols.
- Decoupling capacitors enhance stability and noise immunity for the sensor.
- The design is modular, with flexibility for additional components or configurations (e.g., the NC resistor).